

ANALOG ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.


1. Answer any seven of the following : $2 \times 7 = 14$

- (a) What are the salient features of hybrid parameters?
- (b) How is BJT different from JFET?
- (c) What is intermodulation distortion in amplifier?
- (d) Write down the transfer function of a simple RC low-pass circuit.
- (e) What is the primary function of a phase inverter circuit? Where is it required?
- (f) "Class C amplifier is a voltage-tuned amplifier." Justify.

- (g) What are the sources of thermal noise?
- (h) Why are power transistors provided with heat sinks?
- (i) How are amplifiers classified based on the biasing condition?
- (j) Define stagger-tuned amplifier.

2. (a) Draw the equivalent circuit for the CE and CC configurations subject to the restriction that input is open-circuited. Show that output impedances of the two circuits are identical. 8

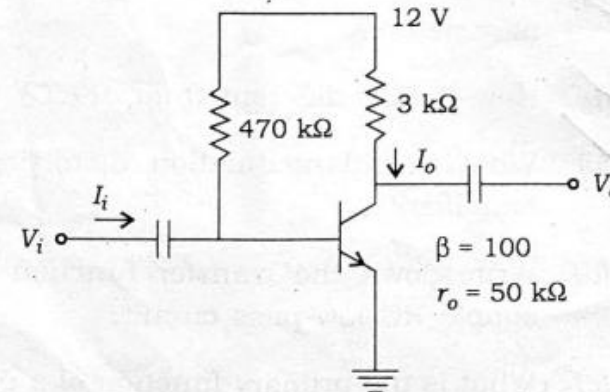(b) For a network shown in the figure below, determine r_e , Z_i , Z_o and A_v : 6



3. (a) Draw the high-frequency π model of a transistor and explain it. 6

(b) Following low-frequency parameters are known for a given transistor at $I_C = 10 \text{ mA}$, $V_{CE} = 10 \text{ V}$ and at room temperature :

$$h_{ie} = 500 \text{ ohms}, \quad h_{re} = 10^{-4}$$

$$h_{oe} = 4 \times 10^{-5} \text{ A/V}, \quad h_{fe} = 100$$

At some operating point, $f_T = 50 \text{ MHz}$ and $C_{ob} = 3 \text{ pF}$. Compute the values of all the hybrid- π parameters. 8

4. (a) Discuss the analysis of emitter follower circuit at high frequencies. 8

(b) In an amplifier, the output power is 1.5 W at 2 kHz and 0.3 W at 20 Hz, while the input power is constant at 10 mW. Determine by how many decibels the gain at 20 Hz is below that at 2 kHz. 6

5. (a) Sketch the response of an amplifier to a low-frequency square wave. Define the term 'tilt'. How is the tilt related with the low 3 dB frequency f_L ? 7

(b) Three identical cascaded stages have an overall upper 3 dB frequency of 20 kHz and a lower 3 dB frequency of 20 Hz. What are f_L and f_H of each stage? Assume non-interacting stages. 7

6. (a) Explain how oscillations are initiated at switch on the system and latter sustained in RC and LC oscillators. 6

(b) Draw the RC phase-shift oscillator circuit using BJT and find the minimum gain required for oscillation and expression for oscillation frequency. 8

7. (a) Derive and explain the Friis transmission formula. 7

(b) Find the maximum effective area of a $\lambda/2$ wire dipole operating at 30 MHz. How much power is received with an incident plane wave of strength 2 mV/m? 7

8. (a) A tank circuit has a capacitor 100 pF and an inductor 100 μH . The resistance of the inductor is 5 Ω . Determine the resonant frequency, impedance at resonance, Q factor and bandwidth of this tank circuit. 7

(b) Show that the maximum conversion efficiency of a class B amplifier is 78.5%. 7

9. Write short notes on any two of the following : 7×2=14

(a) Cascade amplifier

(b) Bootstrapping in emitter follower

(c) Ideal voltage and transresistance amplifiers
